



VHDL




Descrizione Introduttiva

VHDL

- Linguaggio utilizzato per descrivere circuiti digitali


 
- **VHSIC Hardware Description Language**



Very High Speed Integrated Circuits

- Standard IEEE 1987-1991

 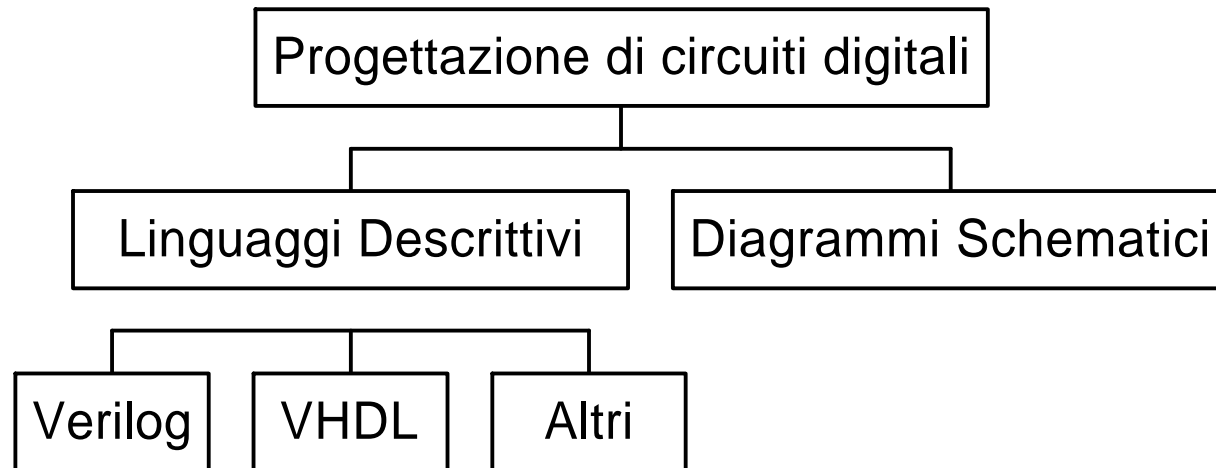VHDL nella progettazione dei circuiti digitali




Caratteristiche principali

- È un linguaggio molto generale
- Permette di descrivere circuiti digitali in vari modi (comportamento, struttura interna, ecc.)
- È supportato dalla maggior parte dei tools di progettazione, simulazione e sintesi automatica
- Alcune istruzioni non sono sintetizzabili dai tools automatici
- È un linguaggio molto esteso



Tipi di descrizioni VHDL

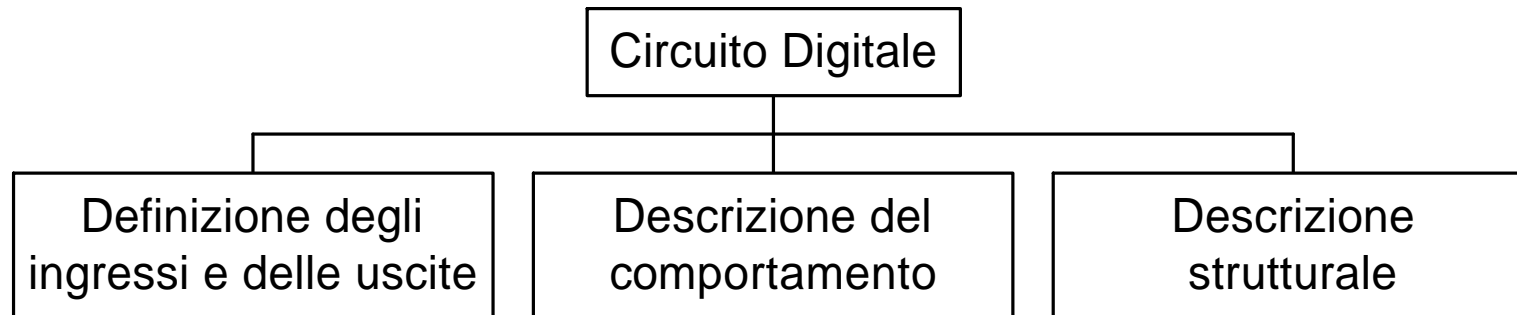

ESEMPIO

In questo esempio si realizzerà una porta XOR utilizzando il linguaggio VHDL.

In particolare si mostreranno la descrizione comportamentale e quella strutturale della porta XOR.


La porta XOR

Tabella della verità

(Comportamento)


a	b	y
0	0	0
0	1	1
1	0	1
1	1	0

Circuito logico

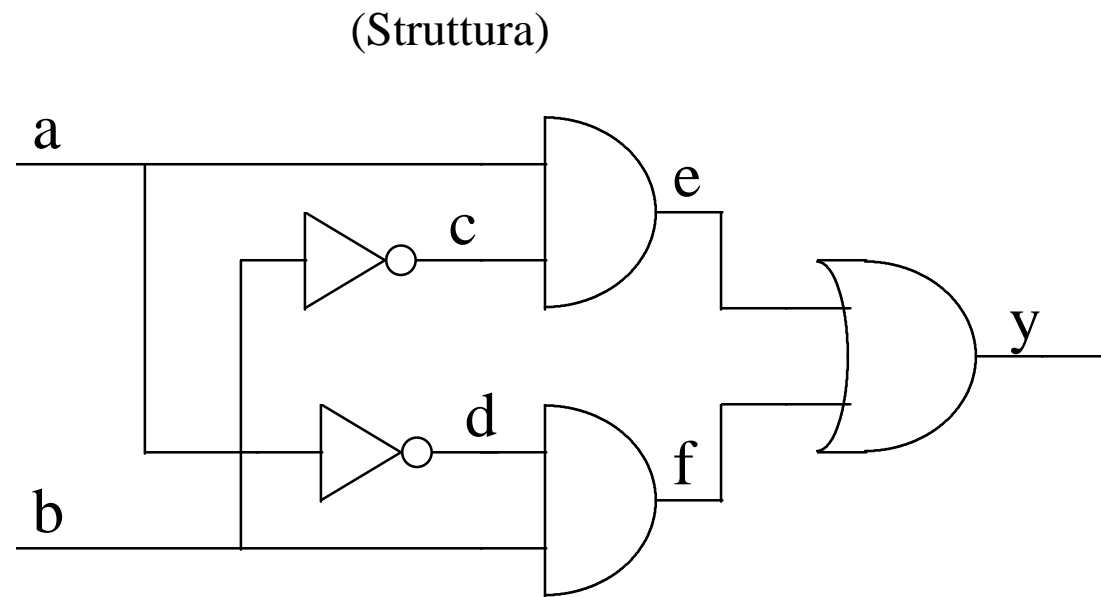


Definizione degli ingressi e delle uscite
 
```
ENTITY xor IS  
  PORT  
  (  
    a : in Bit;  
    b : in Bit;  
    y : out Bit  
  );  
END xor;
```



Descrizione comportamentale (behavioural)
 
```
ARCHITECTURE beh_arch OF xor IS  
BEGIN  
    PROCESS  
    BEGIN  
         $y \leq a \text{ XOR } b;$   
    END PROCESS;  
END beh_arch;
```



Descrizione comportamentale (behavioural)

```
ARCHITECTURE beh_arch OF xor IS
  SIGNAL c : BIT;
  SIGNAL d : BIT;
  SIGNAL e : BIT;
  SIGNAL f : BIT;
BEGIN
  PROCESS
  BEGIN
    c <= NOT b;
    d <= NOT a;
    e <= a AND c;
    f <= b AND d;
    y <= e OR f;
  END PROCESS;
END beh_arch;
```

Descrizione Comportamentale (behavioural)

```
ARCHITECTURE beh_arch OF xor IS
BEGIN
  PROCESS
    VARIABLE c : BIT;
    VARIABLE d : BIT;
    VARIABLE e : BIT;
    VARIABLE f : BIT;
  BEGIN
    c := NOT b;
    d := NOT a;
    e := a AND c;
    f := b AND d;
    y <= e OR f;
  END PROCESS;
END beh_arch;
```

Descrizione strutturale (structural)

```
ARCHITECTURE struc_arch OF xor IS
```

```
    SIGNAL c : BIT;
```

```
    SIGNAL d : BIT;
```

```
    SIGNAL e : BIT;
```

```
    SIGNAL f : BIT;
```

```
COMPONENT      NOT
```

```
    PORT (I : IN BIT; O : OUT BIT);
```

```
END COMPONENT;
```

```
COMPONENT      AND
```

```
    PORT ( I1: IN BIT; I2: IN BIT; O: OUT BIT);
```

```
END COMPONENT;
```

```
COMPONENT      OR
```

```
    PORT ( I1: IN BIT; I2: IN BIT; O: OUT BIT);
```

```
END COMPONENT;
```

(continua)

Descrizione Strutturale (structural)

```
BEGIN
  PROCESS
    BEGIN
      u1: NOT( b => I , c => O );
      u2: NOT( a => I , d => O );
      u3: AND( a => I1 , c => I2 , e => O );
      u4: AND( b => I1 , d => I2 , f => O );
      u5: OR( e => I1 , f => I2 , y => O );
    END PROCESS;
  END struc_arch;
```

Librerie di componenti

```
USE ieee.std_logic_1164.ALL;
```

```
USE logic.ALL
```

```
ENTITY xor IS
```

```
...
```

```
END xor;
```

```
ARCHITECTURE arch OF xor IS
```

```
BEGIN
```

```
...
```

```
END arch;
```



Tipi di Dati Standard

- BIT

Dato il cui valore è '0' o '1'

```
SIGNAL dato : BIT;
```

```
dato <= '0';
```



- INTEGER

Numero compreso fra -2147483648 e 2147483647

```
SIGNAL dato : INTEGER;
```

```
dato <= 18;
```

Tipi di Dati Standard

- REAL

Numero compreso fra -1×10^{38} e 1×10^{38} con almeno 16 cifre significative

```
SIGNAL dato : REAL;  
dato <= 1.24;
```

- BOOLEAN

Dato il cui valore è FALSE o TRUE

```
VARIABLE dato : BOOLEAN;  
dato := '0';
```


Tipi di Dati Standard

- CHARACTER

Un qualunque carattere ASCII

```
VARIABLE dato : CHARACTER;
```

```
dato := 'A';
```

Dati di Libreria

La libreria standard “ieee.std_logic_1164”
aggiunge ai dati standard i seguenti tipi di dati
elementari:

- **STD_LOGIC**

Dato il cui valore è ‘0’, ‘1’, ‘Z’, ‘X’

```
SIGNAL dato : STD_LOGIC;
```

```
dato <= '1';
```

Dati di Libreria

- **STD_LOGIC_VECTOR**

Vettore di dati tipo STD_LOGIC

```
SIGNAL dato : STD_LOGIC_VECTOR(7 downto 0);
```

```
dato <= '110X11Z0';
```

```
dato(4 DOWNTO 2) <= 'X11';
```

```
dato(7 DOWNTO 6) <= dato(1 DOWNTO 0);
```

- **SIGNED, UNSIGNED**

Vettori di bit che rappresentano numeri

```
SIGNAL dato : UNSIGNED;
```

```
dato <= 18;
```

Struttura generale di un programma

USE *libreria*

ENTITY *circuito* IS

...

END *circuito*;

ARCHITECTURE *arch* OF *circuito* IS

SIGNAL *signal_globali*

BEGIN

PROCESS

SIGNAL *signal_locali*

VARIABLE *variabili_locali*

BEGIN

...

END PROCESS;

PROCESS

...

END PROCESS;

END *arch*;



Confronto fra Variable e Signal

SIGNAL


- Un nuovo valore viene aggiornato dopo un ritardo predefinito
- Ci sono SIGNAL locali ai PROCESS e globali alla ARCHITECT
- Rappresentano i fili di collegamento fra componenti

VARIABLE

- Un nuovo valore viene aggiornato immediatamente
- Ci sono VARIABLE soltanto locali ai PROCESS
- Non hanno nessuna rappresentazione

Controllo dei processi: IF-THEN-ELSE
 
```
PROCESS
  SIGNAL a : STD_LOGIC;
  SIGNAL y : STD_LOGIC;
  SIGNAL enable : STD_LOGIC;
BEGIN
  IF (enable = '1') THEN
    y <= a;
  ELSE
    y <= '0';
  END IF;
END PROCESS;
```



Controllo dei processi: IF-THEN-ELSE

PROCESS

```
SIGNAL a : STD_LOGIC_VECTOR(2 downto 0);  
SIGNAL y : STD_LOGIC_VECTOR(2 downto 0);  
SIGNAL enable : STD_LOGIC;
```

BEGIN

```
IF (enable = '1') THEN
```


```
    y <= a;
```

```
ELSE
```

```
    y <= '0';
```


```
END IF;
```

```
END PROCESS;
```

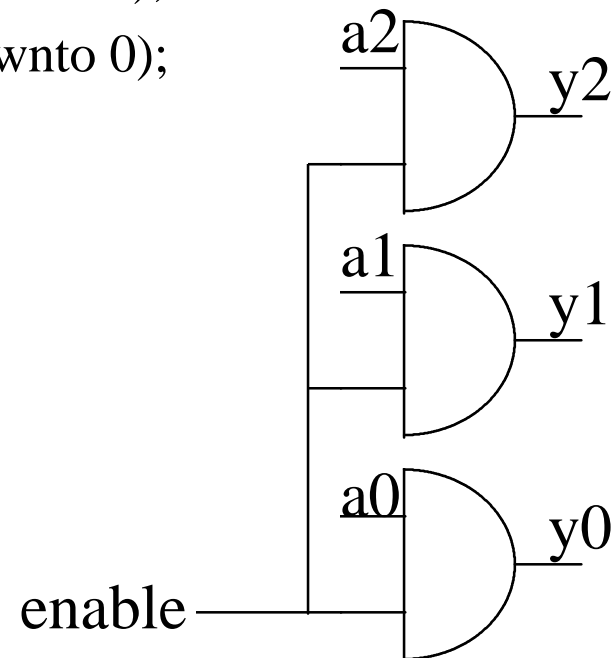

Controllo dei processi: IF-THEN-ELSE
 
```
PROCESS  
    SIGNAL a : STD_LOGIC;  
    SIGNAL y : STD_LOGIC;  
    SIGNAL enable : STD_LOGIC;  
BEGIN  
    IF (enable = '1') THEN  
        y <= NOT a;  
    ELSE  
        y <= 'Z';  
    END IF;  
END PROCESS;
```



Controllo dei processi: IF-THEN-ELSIF-ELSE

PROCESS

SIGNAL a : STD_LOGIC;

SIGNAL y : STD_LOGIC;

SIGNAL enable : STD_LOGIC_VECTOR(1 downto 0);

BEGIN

IF (enable = '00') THEN

 y <= a;

ELSIF (enable = '01' OR enable = '10') THEN

 y <= '0';

ELSE

 y <= '1';

END IF;

END PROCESS;

Controllo dei processi: CASE

```
PROCESS
```

```
    SIGNAL a : STD_LOGIC;
```

```
    SIGNAL y : STD_LOGIC;
```

```
    SIGNAL enable : STD_LOGIC_VECTOR(1 downto 0);
```

```
BEGIN
```

```
    CASE enable IS
```

```
        WHEN '00' =>
```

```
            y <= a;
```

```
        WHEN '01' =>
```

```
            y <= '0';
```

```
        WHEN '10' =>
```

```
            y <= '0';
```

```
        WHEN OTHERS =>
```

```
            y <= '1';
```

```
    END CASE;
```

```
END PROCESS;
```

Controllo dei processi: CASE

```
PROCESS
```

```
    SIGNAL y : STD_LOGIC_VECTOR(3 downto 0);
```

```
    SIGNAL a : STD_LOGIC_VECTOR(1 downto 0);
```

```
BEGIN
```

```
    CASE a IS
```

```
        WHEN '00' =>
```

```
            y <= '0001';
```

```
        WHEN '01' =>
```

```
            y <= '0010';
```

```
        WHEN '10' =>
```

```
            y <= '0100';
```


```
        WHEN '11' =>
```

```
            y <= '1000';
```

```
        WHEN OTHERS => ;
```


```
    END CASE;
```

```
END PROCESS;
```

 



Controllo dei processi: SELECT
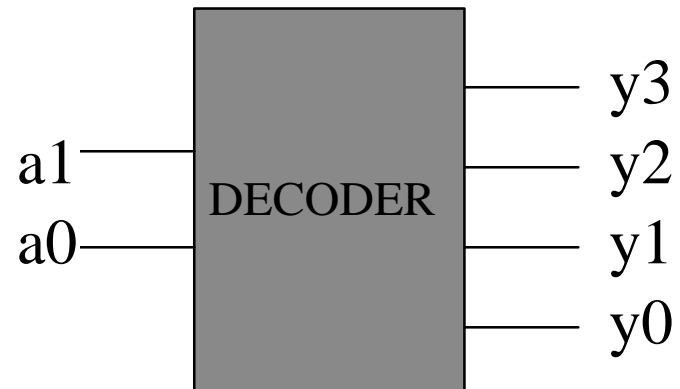
```
PROCESS
  SIGNAL y : STD_LOGIC_VECTOR(3 downto 0);
  SIGNAL a : STD_LOGIC_VECTOR(1 downto 0);
BEGIN
  WITH a SELECT
    y <= '0001' WHEN '00',
         '0010' WHEN '01',
         '0100' WHEN '10',
         '1000' WHEN '11';
END PROCESS;
```




Circuiti Sequenziali: FF-D
 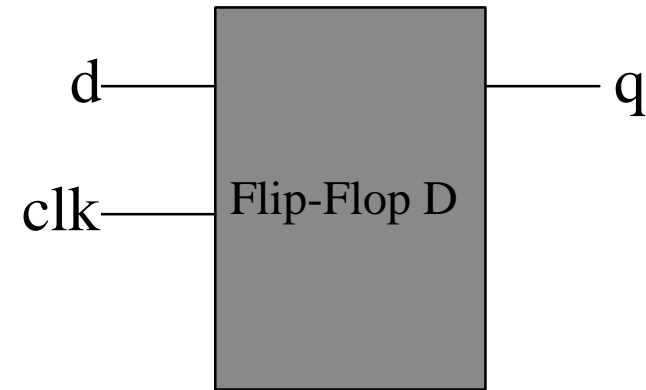
```
ARCHITECTURE arch OF ffd IS
  SIGNAL d : STD_LOGIC;
  SIGNAL q : STD_LOGIC;
  SIGNAL clk : STD_LOGIC;
BEGIN
  PROCESS(clk)
  BEGIN
    IF (clk'EVENT AND clk = '1') THEN
      q <= d;
    END IF;
  END PROCESS;
END arch;
```



Circuiti Sequenziali: FF-D con RESET
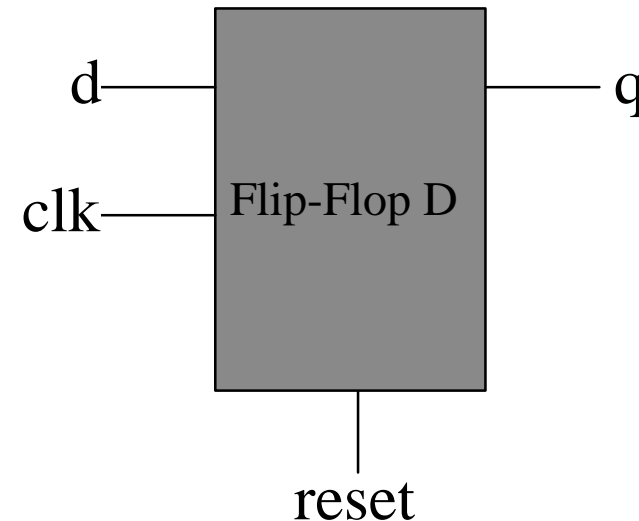
```
ARCHITECTURE arch OF ffd IS
  SIGNAL d : STD_LOGIC;
  SIGNAL q : STD_LOGIC;
  SIGNAL clk : STD_LOGIC;
  SIGNAL reset : STD_LOGIC;
BEGIN
  PROCESS(clk, reset)
  BEGIN
    IF (reset = '1') THEN
      q <= '0';
    ELSIF (clk'EVENT AND clk = '1') THEN
      q <= d;
    END IF;
  END PROCESS;
END arch;
```



Registro di scorrimento

```
ARCHITECTURE arch OF shift IS
```

```
  SIGNAL d : STD_LOGIC;
```

```
  SIGNAL q : STD_LOGIC_VECTOR(7 downto 0);
```

```
  SIGNAL clk : STD_LOGIC;
```

```
  SIGNAL reset : STD_LOGIC;
```

```
BEGIN
```

```
  PROCESS(clk, reset)
```

```
  BEGIN
```

```
    IF (reset = '1') THEN
```

```
      q <= '00000000';
```

```
    ELSIF (clk'EVENT AND clk = '1') THEN
```


```
      q(0) <= d;
```

```
      q(7 downto 1) <= q(6 downto 0);
```

```
    END IF;
```


```
  END PROCESS;
```

```
END arch;
```

 

Contatore
 
```
ARCHITECTURE arch OF counter IS
    SIGNAL q : UNSIGNED(7 downto 0);
    SIGNAL clk : STD_LOGIC;
    SIGNAL reset : STD_LOGIC;
BEGIN
    PROCESS(clk, reset)
    BEGIN
        IF (reset = '1') THEN
            q <= '00000000';
        ELSIF (clk'EVENT AND clk = '1') THEN
            q <= q + 1;
        END IF;
    END PROCESS;
END arch;
```



Sommatore

```
ARCHITECTURE arch OF adder IS
    SIGNAL d1 : SIGNED(7 downto 0);
    SIGNAL d2 : SIGNED(7 downto 0);
    SIGNAL y : SIGNED(8 downto 0);
    SIGNAL clk : STD_LOGIC;
    SIGNAL reset : STD_LOGIC;
BEGIN
    PROCESS(clk, reset)
    BEGIN
        IF (reset = '1') THEN
            y <= '000000000';
        ELSIF (clk'EVENT AND clk = '1') THEN
            y <= d1 + d2;
        END IF;
    END PROCESS;
END arch;
```


$$1+1=3$$




Attenzione agli errori!!

(o errori?)
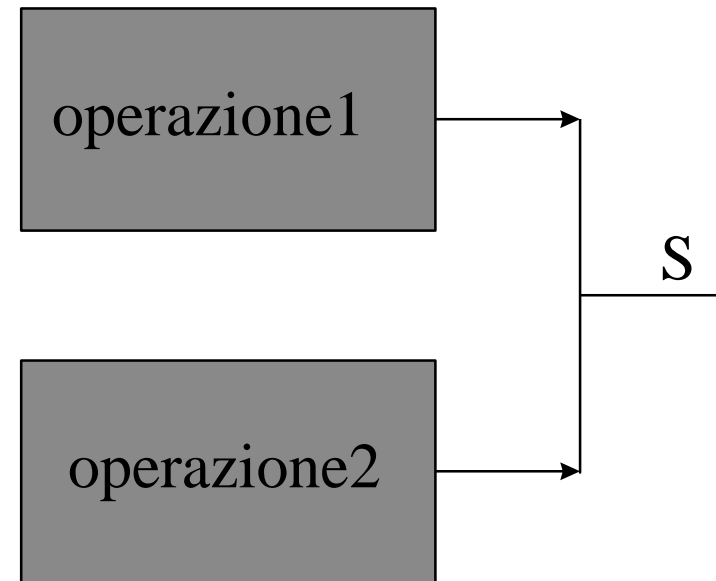
```
ARCHITECTURE arch OF circ IS  
SIGNAL s : BIT;  
BEGIN  
  PROCESS  
  BEGIN  
    s <= operazione1;  
  END PROCESS;  
  
  PROCESS  
  BEGIN  
    s <= operazione2;  
  END PROCESS;  
END arch;
```



Macchina a stati finiti (FSA)

 

Macchina a stati finiti (FSA)

```
ENTITY fsm IS
```

```
  PORT
```

```
  (
```

```
    clk : IN STD_LOGIC;
```

```
    reset : IN STD_LOGIC;
```

```
    a, b : IN STD_LOGIC;
```

```
    q : OUT STD_LOGIC
```

```
  );
```

```
END fsm;
```

```
ARCHITECTURE arch OF fsm IS
```

```
  TYPE STATE_TYPE IS (s1, s2, s3);
```

```
  SIGNAL stato: STATE_TYPE;
```

```
BEGIN
```

```
  PROCESS (clk)
```

```
BEGIN
```

```
  IF reset = '1' THEN
```

```
    stato <= s1;
```

```
  ELSIF clk'EVENT AND clk = '1' THEN
```

```
    CASE stato IS
```

```
      WHEN s1 =>
```

```
        IF (NOT a) THEN
```

```
          stato <= s2;
```

```
        END IF;
```

```
      WHEN s2 =>
```

```
        IF (b) THEN
```

```
          stato <= s1;
```

```
        ELSIF (a) THEN
```

```
          stato <= s3;
```

```
        END IF;
```

Macchina a stati finiti (FSA)

```
WHEN s3 =>  
  IF (NOT b) THEN  
    stato <= s1;  
  ELSIF (a AND b) THEN  
    stato <= s2;  
  END IF;  
END CASE;  
END IF;  
END PROCESS;  
  
WITH state SELECT  
  q <= '0' WHEN s1,  
  '0' WHEN s2,  
  '1' WHEN s3;  
END arch;
```



Bibliografia

VHDL: Hardware Description and Design

Roger Lipsett

Carl Schaefer

Cary Ussery

Kluwer Academic Publisher

Bib. Elettronica L4 - 58

